

## Experiment: VI Characteristics of Diode

**Aim:** To plot VI characteristics of a PN junction diode

**Apparatus:** Using Virtual Lab (<http://vlabs.iitkgp.ernet.in/be/>)

### Theory:

The diode is a device formed from a junction of n-type and p-type semiconductor material. The lead connected to the p-type material is called the anode and the lead connected to the n-type material is the cathode. In general, the cathode of a diode is marked by a solid line on the diode.



Figure 1 PN junction diode structure

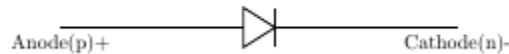


Figure 2 PN junction diode symbol

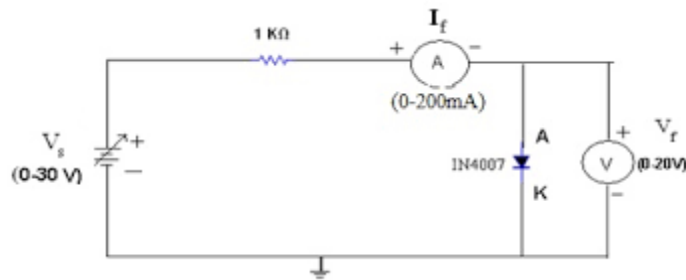


Figure 3 Circuit diagram for VI characteristics of diode

In forward biasing, the positive terminal of battery is connected to the P side and the negative terminal of battery is connected to the N side of the diode. Diode will conduct in forward biasing because the forward biasing will decrease the depletion region width and overcome the barrier potential. In order to conduct, the forward biasing voltage should be greater than the barrier potential. During forward biasing the diode acts like a closed switch with a potential drop of nearly 0.6 V across it for a silicon diode. The forward and reverse bias characteristics of a silicon diode. From the graph, you may notice that the diode starts conducting when the forward bias voltage exceeds around 0.6 volts (for Si diode). This voltage is called cut-in voltage.

In reverse biasing, the positive terminal of battery is connected to the N side and the negative terminal of battery is connected to the P side of a diode. In reverse biasing, the diode does not conduct electricity, since reverse biasing leads to an increase in the depletion region width; hence

current carrier charges find it more difficult to overcome the barrier potential. The diode will act like an open switch and there is no current flow.

### Procedure:

**Forward Biased:** ([http://vlabs.iitkgp.ernet.in/be/exp5/forwardbiaseddiode\\_si\\_ver1.html](http://vlabs.iitkgp.ernet.in/be/exp5/forwardbiaseddiode_si_ver1.html) )

1. Set DC voltage to 0.2 V .
2. Select the diode.
3. Set the resistor to 1k
4. Voltmeter is placed parallel to Silicon diode and ammeter series with resistor.
5. The positive side of battery to the P side(anode) and the negative of battery to the N side(cathode) of the diode.
6. Now vary the voltage upto 5V and note the Voltmeter and Ammeter reading for particular DC voltage.
7. Take the readings and note Voltmeter reading across Silicon diode and Ammeter reading.
8. Plot the V-I graph and observe the change.

**Reverse Biased:** ([http://vlabs.iitkgp.ernet.in/be/exp5/reversebiaseddiode\\_si\\_ver1.html](http://vlabs.iitkgp.ernet.in/be/exp5/reversebiaseddiode_si_ver1.html) )

1. Set DC voltage to 0.2 V .
2. Select the diode.
3. Set the resistor.
4. Voltmeter is placed parallel to Silicon diode and ammeter series with resistor.
5. The positive terminal of battery is connected to the N side(cathode) and the negative terminal of battery is connected to the P side(anode) of a diode.
6. Now vary the voltage upto 30V and note the Voltmeter and Ammeter reading for DC voltage.
7. Take the readings and note Voltmeter reading across Silicon diode and Ammeter reading.
8. Plot the V-I graph and observe the change.

### Observation Table

S.No.	Input DC voltage	Forward Voltage	Forward Current

S.No.	Input DC voltage	Reverse Voltage	Reverse Current

**Circuit Diagram (on Vlab, paste here):**

**VI Characteristics of PN junction diode:**

**Conclusion:**