

## Tutorial - 3

1)

$V_B = 4V$

$\beta = 100$

$V_E = ?$ ,  $\alpha = ?$ ,  $R_E = ?$

~~2.1~~~~2.2~~

$V_{BE} = 0.7V$

2eq  $\rightarrow$  Voltage divider bias

$$\frac{R_2}{R_1 + R_2} \times V_{CC} = 4$$

$$R_1 + R_2 = \frac{12}{0.1 \text{ mA}}$$

$R_2 = 40K$

$R_1 = 80K$

$$\frac{R_2}{R_1 + R_2} = \frac{4}{12} = \frac{1}{3}$$

$R_1 + R_2 = 3R_2$

$\Rightarrow R_1 = 2R_2$

$$I_C = \alpha I_E$$
$$= (\beta + 1) I_E = (\beta + 1) I_B$$
$$= 101 I_B$$

$$V_{BE} = V_B - V_E \Rightarrow V_E = 3.3V$$

$V_E = I_E R_E$

$\Rightarrow R_E = 3.3\Omega$

$$R_C = V_{CC} - V_{CE} - I_E R_E = 12 - 0.7 - 3.3$$
$$= \underline{8\Omega}$$

2)

$V_{CC} = 5V$

$V_{BE} = 0.7V$

Fig 2  $\rightarrow$  ON, Fig 3  $\rightarrow$  OFF

$V_{CC} = V_{CE} + I_E R_L + (10K) I_B$


$\Rightarrow 5 = (V_B - V_E) + (1+100) I_B R_L + (10K) I_B$

$\Rightarrow 5 = 101 I_B + V_B - V_E + 10I_B$


$\Rightarrow 5 - 0.7 = 111 I_B$

$\Rightarrow \frac{4.3}{111} = I_B$

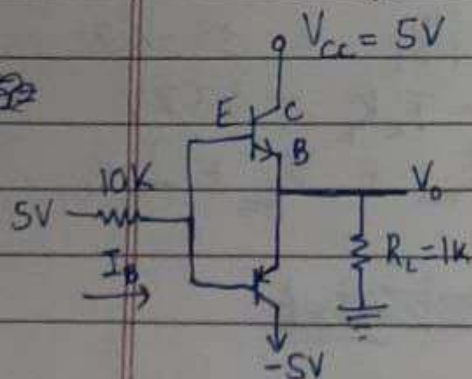$\Rightarrow \underline{0.039 \text{ mA}} = I_B$


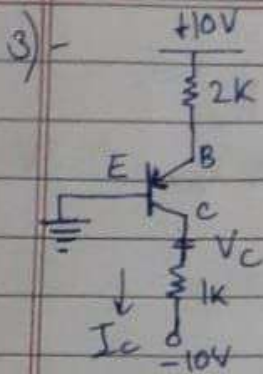
$$V_o = (1 + \beta) I_B R_L$$
$$\Rightarrow \underline{V_o = 3.939V}$$



$$V_E = V_B = 0.7$$


$$\Rightarrow I_E = \frac{10 - 0.7}{2} = 4.65 \text{ mA}$$

$$\alpha = \frac{1 + \beta}{\beta} \Rightarrow \alpha = 0.99$$

$$I_c = \alpha I_E = 4.6035 \text{ mA}$$

$$V_c - 4.6035 = -10$$
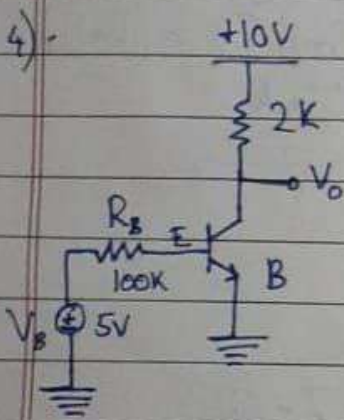
$$\Rightarrow V_c = \underline{\underline{-5.3965 \text{ V}}}$$



$$V_B - I_B R_B - V_{BE} = 0$$

$$5 - I_B (100) - 0.7 = 0$$


$$\Rightarrow I_B = \underline{\underline{0.043}}$$

$$I_c = \beta I_B = 4.3 \text{ mA}$$

$$10 - I_c R_c = V_c$$

$$10 - 4.3 \times 2 = V_c = 1.4 \text{ V}$$
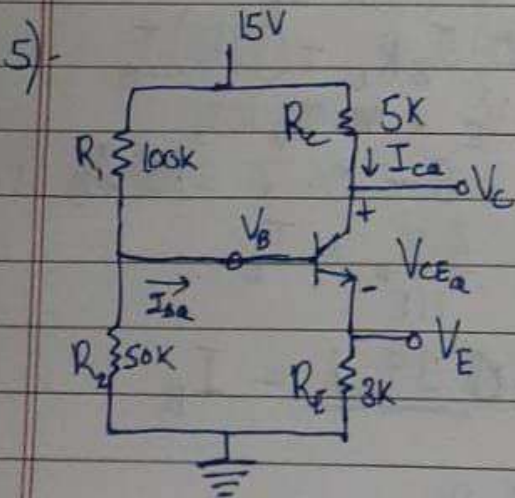
$$I_E = (1 + \beta) I_B \Rightarrow I_E = \underline{\underline{4.343 \text{ V}}}$$



$$\beta = 100$$

$$V_{BB} = \frac{15 \times R_2}{R_1 + R_2} = 5 \text{ V}$$

$$R_{net} = R_1 \parallel R_2 = 33.3 \text{ K}\Omega$$

$$V_B = V_{BE} - I_E R_E = 4.57 \text{ V}$$

$$\Rightarrow V_{BB} = I_B R_{net} + V_{BE} + I_E R_E$$

$$\underline{\underline{I_B = 1.28 \text{ mA}}}$$



$$V_{BB} - I_B R_{net} - V_{BE} - 3I_E = 0$$

$$\Rightarrow I_E = (1 + \beta) I_B = 101 I_B$$

$$5 - 33.3 \text{ k} I_B - 0.7 - 3 \text{ k} (101 I_B) = 0$$

$$4.7 = (303 + 33.3) \text{ k} I_B$$

$$I_B = \frac{4.7 \text{ mA}}{336.3} = 0.014 \text{ mA}$$

$$I_E = 101 I_B = 1.414 \text{ mA}$$

$$I_C = \beta I_B = 1.4 \text{ mA}$$

$$V_B = V_{BB} - I_B R_{net} = 5 - (0.014 \text{ mA})(33.3 \text{ k}) = 4.5 \text{ V}$$


$$V_E = I_E R_E = 15 \text{ k} \times 1.414 \text{ mA} = 21.2 \text{ V}$$

$$15 - I_C (45 \text{ k}) - V_{CE} - I_E (3 \text{ k}) = 0$$

$$\Rightarrow V_{CE} = -21.21 - 7 + 15 = -13.21 \text{ V}$$

$$V_C = I_C R_C = 1.4 \text{ mA} \times 5 \text{ k} = 7 \text{ V}$$

6)-

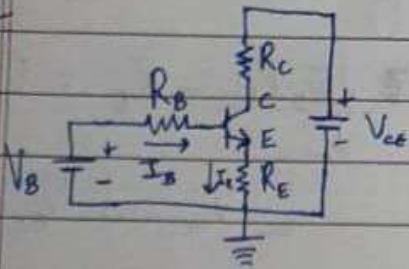

The extent to which collector current  $I_C$  is stabilised with varying  $I_{C0}$  is measured by stabilising factors. It is defined as the rate of change of collector current  $I_C$  w.r.t. collector base leakage current  $I_{C0}$ , keeping both the current  $I_B$  and current gain  $\beta$  constant. The collector current for a CE amplifier is given by -

$$I_C = \beta I_B + (1 + \beta) I_{C0}$$

$$\text{Diff.} \Rightarrow 1 = \frac{\beta dI_B}{dI_C} + (1 + \beta) \frac{dI_{C0}}{dI_C}$$


$$\Rightarrow S = \frac{1 + \beta}{1 - \beta \frac{dI_B}{dI_C}}$$

$$\text{for self bias, } S = \frac{(1 + \beta) \left(1 + \frac{R_B}{R_E}\right)}{1 + \beta + \frac{R_B}{R_E}}$$

The stability factor  $S'$  is defined as the rate of change of  $I_C$  with

$V_{BE}$ , keeping  $I_{CQ}$  and  $V_{BE}$  constant.  
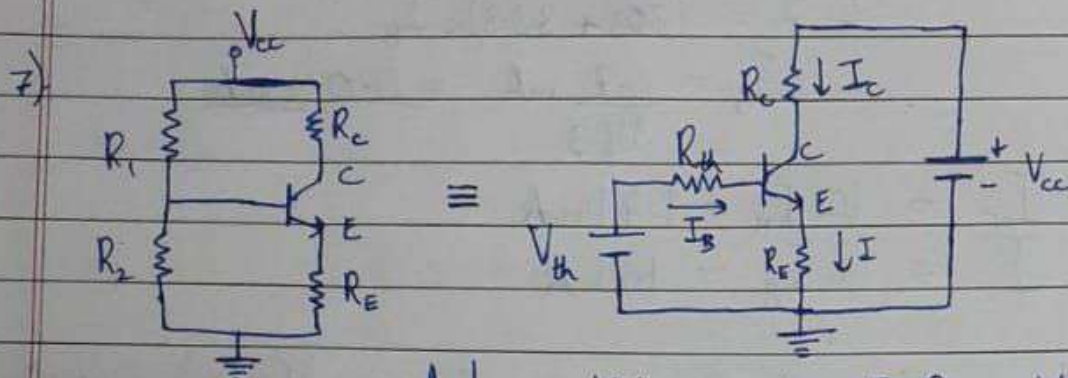
$$S' = \frac{\partial I_C}{\partial V_{BE}}$$



Applying KVL,  $V_{th} - I_B R_{th} - V_{BE} - I_E R_E = 0$   

$$I_B = \frac{V_{th} - V_{BE}}{R_{th} - (1+\beta)R_E} \quad \text{--- (1)}$$

$$I_E = \frac{V_{th} - V_{BE}}{\frac{R_{th}}{1+\beta} + R_E} \approx I_C \quad (\because I_E \approx I_C)$$

$$V_{th} - I_B R_{th} - V_{BE} - (I_B + I_C) R_E = 0$$

diff.  $\Rightarrow 0 - \frac{dI_B}{dI_C} R_{th} - 0 - \frac{dI_B}{dI_C} R_E - R_E = 0$

$[\because V_{th} \text{ and } V_{BE} \text{ are constants}]$

$$\frac{dI_B}{dI_C} R_{th} + \frac{dI_B}{dI_C} R_E + R_E = 0$$

$$\Rightarrow \frac{dI_B}{dI_C} = \frac{-R_E}{R_{th} + R_E}$$

$$\Rightarrow S = \frac{1+\beta}{1-\beta \left( \frac{dI_B}{dI_C} \right)} = \frac{1+\beta}{1+\beta \left( \frac{R_E}{R_{th}+R_E} \right)}$$