



Thapar Institute of Engineering and Technology (Deemed to be University)
DEPARTMENT OF ELECTRICAL AND INSTRUMENTATION ENGINEERING

TUTORIAL 1 (BASIC LAWS)

UES 013 ELECTRICAL AND ELECTRONICS ENGINEERING

FIRST YEAR (CSE)

Course Instructor: Dr. Shakti Singh

1. Use the KVL and KCL method to find how much power the 20-V source extracts from the circuit in Fig (60W)

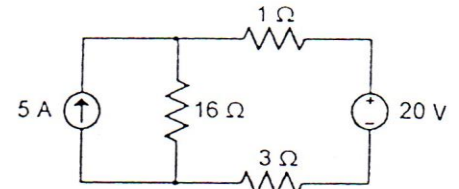


Figure 1

2. Referring to Figure 2
- Using KVL and KCL, find the branch currents i_a through i_e in the circuit.
 - Find the total power developed in the circuit.
- (ans: a) 5.6 A, 0.6 A, 5 A, 0.2 A, 4.8 A b) 2048 W

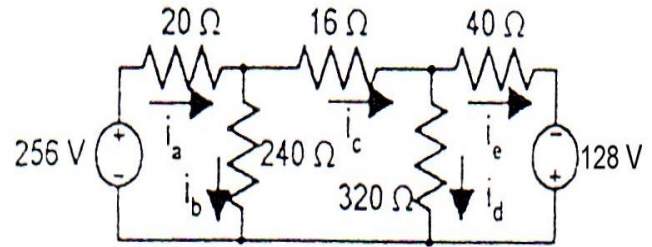


Figure 2

3. Using KCL and KVL Analysis, find v in Fig 3. (20 V)

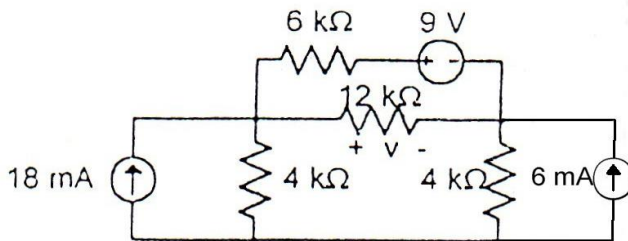


Figure 3

4. Find current in 100 ohms resistor in Figure 4, using KVL and KCL.

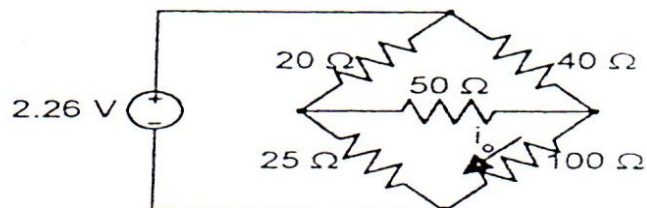


Figure 4



Thapar Institute of Engineering and Technology (Deemed to be University)
DEPARTMENT OF ELECTRICAL AND INSTRUMENTATION ENGINEERING

TUTORIAL 2 (NODAL & MESH ANALYSIS)

UES 013 ELECTRICAL AND ELECTRONICS ENGINEERING

FIRST YEAR (CSE)

Course Instructor: Dr. Shakti Singh

Q1. Use the node-voltage method to find how much power the 20-V source extracts from the circuit in Fig 1 (60W)

Q2. Use the node-voltage method to find v_1 and v_2 in Fig 2 (100 V, 50 V)

Q3. Use the node-voltage method to find the power delivered by the dependent voltage source in Fig 3. (Ans: -750W)

Q4. Find v and i in Fig 4 using Nodal Analysis.
(ans : 0.46V, 2.23A)

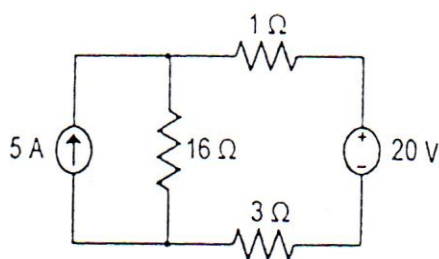


Figure 1

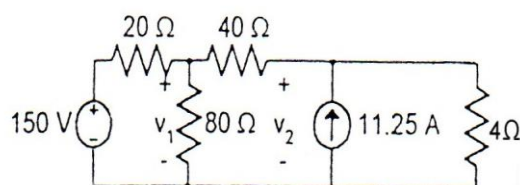


Figure 2

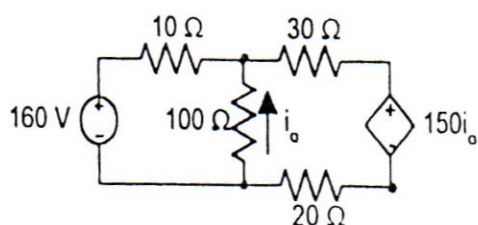


Figure 3

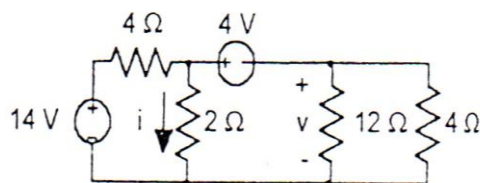


Figure 4

Q5. Using mesh analysis finds mesh currents in Figure 3 and 4.

Q6. Use Mesh analysis to find the power dissipated in the 1Ω resistor. (Ans: 36W)

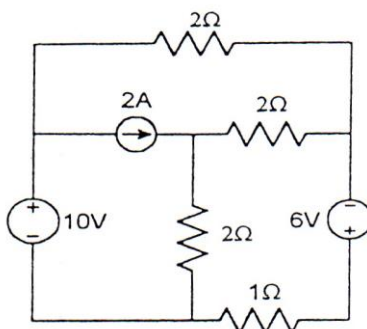


Figure 6



Thapar Institute of Engineering and Technology (Deemed to be University)
DEPARTMENT OF ELECTRICAL AND INSTRUMENTATION ENGINEERING

TUTORIAL 3, 4 (CIRCUIT THEOREMS)

UES 013 ELECTRICAL AND ELECTRONICS ENGINEERING

FIRST YEAR (CSE)

Course Instructor: Dr. Shakti Singh

Superposition

1. Using Superposition theorem (figure 1) , find the current I in 16Ω . (2A)
2. Using Superposition (Figure 2), find the voltage, V . (32 V)

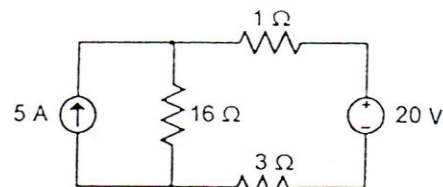


Figure 1

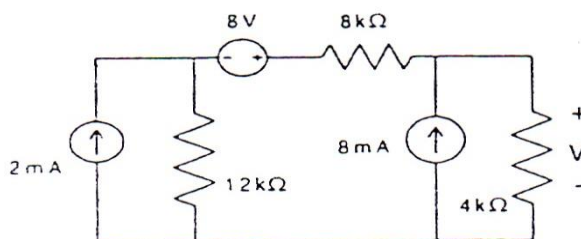


Figure 2

Thevenin Theorem

3. Find the Thevenin equivalent circuit with respect to terminal ab for figure 3. (60 V, 10Ω)

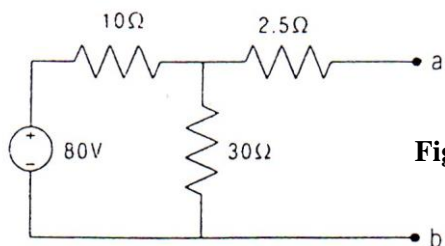


Figure 3

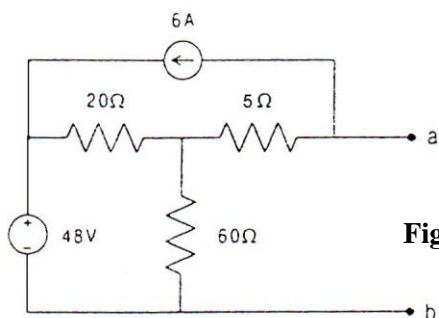


Figure 4

4. Find the Thevenin equivalent circuit with respect to terminal ab for figure 4. (-84 V, 20Ω)
5. Find the Thevenin equivalent circuit with respect to terminal ab for figure 5. (30 V, 20Ω)

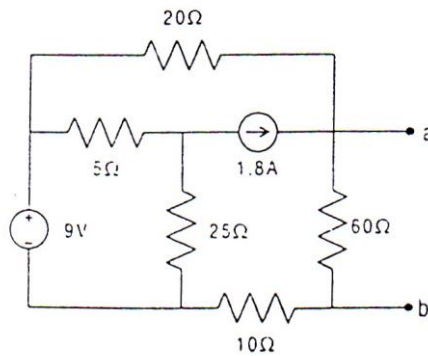


Figure 5

Norton Theorem

6. Find the Norton equivalent circuit with respect to terminals ab for figure 6 . (- 4 mA, 4 kΩ)

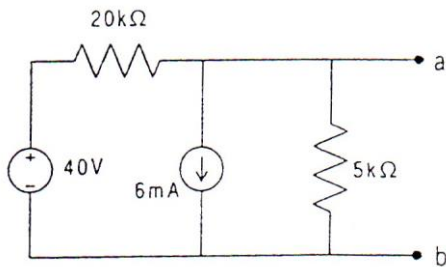


Figure 6

7. Find the Norton equivalent circuit with ab for figure 7. (1.67 A, 2.4 Ω)

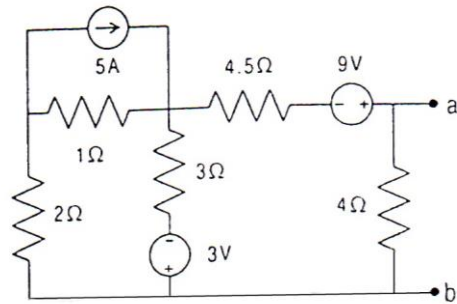


Figure 7

respect to terminals

Source-Transformation (Thevenin & Norton)

8. Find the Thevenin and Norton equivalent for the network shown below.
 ((i) -22.65V, - 15.95A, 1.42 Ω (ii) 73 V, 6.64A, 11 Ω)
 (i) (ii)

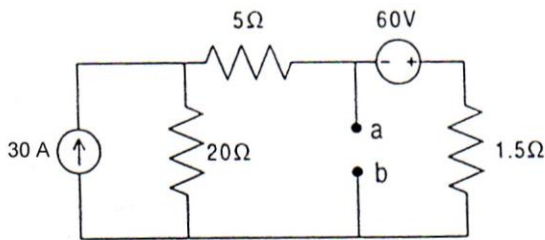


Figure8(i)

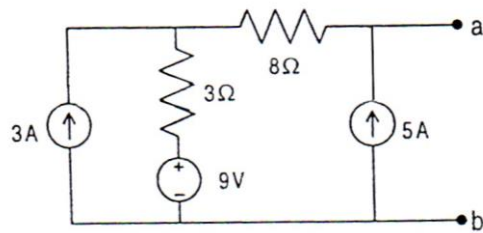


Figure 8(ii)

Maximum Power Transfer

9. The load resistance in figure below is adjusted until maximum power is delivered. Find the power delivered and the value of R_L .

((i) $600\ \Omega$, $38.4\ \text{mW}$ (ii) $21.7\ \Omega$, $0.8\ \text{W}$)

(i) (ii)

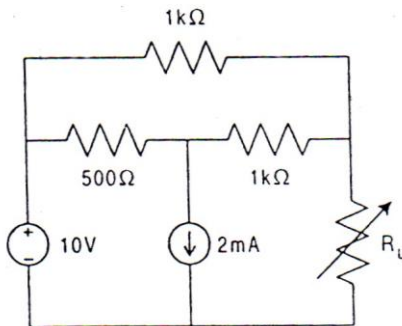


Figure 9(i)

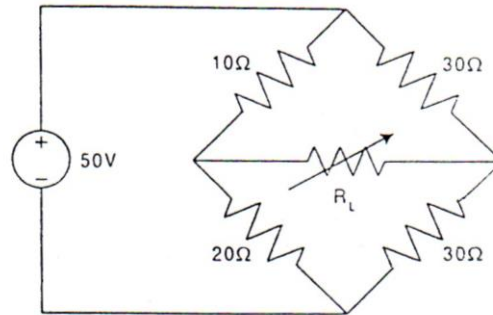


Figure 9(ii)



Thapar Institute of Engineering and Technology (Deemed to be University)
DEPARTMENT OF ELECTRICAL AND INSTRUMENTATION ENGINEERING

TUTORIAL 5 (THEOREMS)

UES 013 ELECTRICAL AND ELECTRONICS ENGINEERING

FIRST YEAR (CSE)

Course Instructor: Dr. Shakti Singh

1. Calculate the effective resistance between points A and B as given in Fig. 1. [Ans. 3.69Ω]
2. In the circuit shown in Fig. 2, calculate current through 1Ω resistance connected between A-B, using Thevenin's theorem. Verify your answer using superposition theorem. [Ans. 14 A]
3. For the circuit shown in Fig. 3, find the voltage across 4Ω resistance by source transformation. [Ans. 7.112 V]
4. Using superposition theorem, find the value of output voltage V_0 in the circuit of Fig. 4. [Ans. 2 V]
5. Determine the Thevenin's equivalent circuit as viewed from the open-circuit terminals a and b of the network shown in Fig. 5. All resistances are in ohms. [Ans. $V_{oc} = 3 \text{ V}$, $R_{TH} = 5 \Omega$]
6. Find i_0 in the circuit of Fig. 6 using superposition theorem. [Ans. $i_0 = -0.4706 \text{ A}$]

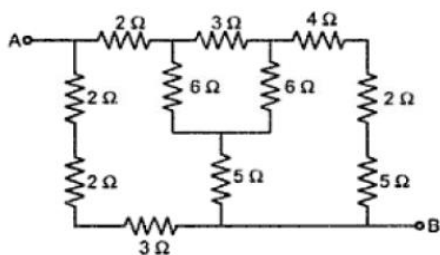


Fig. 1

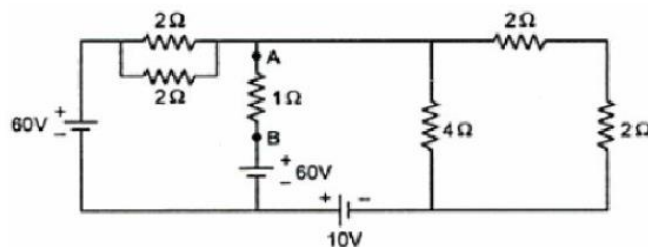


Fig. 2

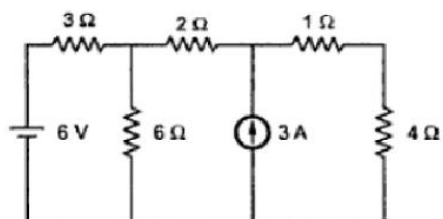


Fig. 3

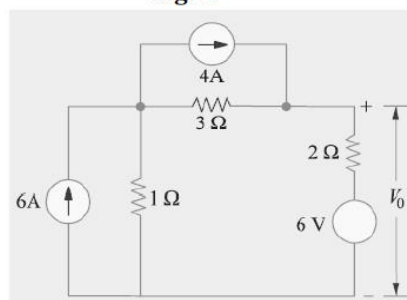


Fig. 4

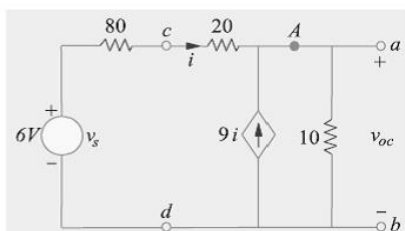


Fig. 5

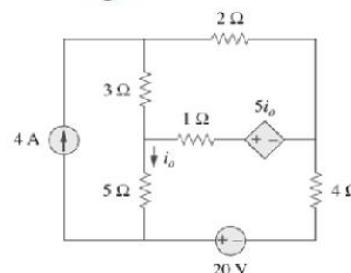


Fig. 6