

Experiment: Single Phase AC Series Circuit

Ayush Nagpure

Batch – 2024

Application No - 158377


Subgroup – 1H3

Objectives: To determine experimentally;

- (1) Voltage distribution in a single phase AC series circuit.
- (2) Power and power factor of the (a) circuit (b) choke coil.
- (3) The value of the circuit elements R, L & C

Equipments: (1) Resistor (2) Choke coil (3) Capacitor (4) SPDT Key

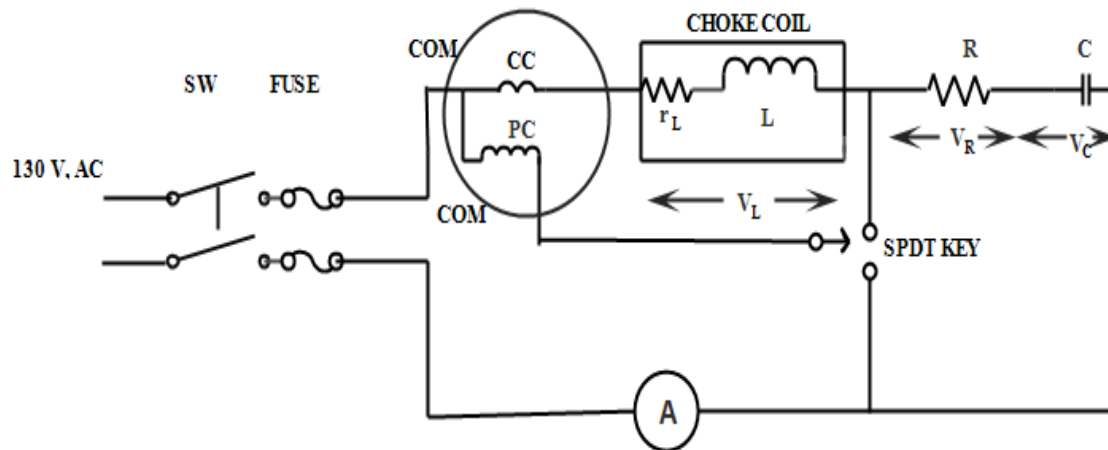(5) Wattmeter 250V/1Amp (6) AC volt-meter 150V (7) AC Ammeter- 1Amp



Circuit Diagram

Theory:

For a given AC series circuit, when energized from an ac source, same current flows through series connected resistance R, choke coil L & capacitor C.

The voltage drop across these elements is as follows:

- (1) Across Resistance; $V_R = IR$
- (2) Across Inductance; $V_L = IX_L = I(j\omega L)$
- (3) Across Capacitor; $V_C = -jIX_C = I/(j\omega C)$
- (4) The resistance of inductance r_L can be measured by multimeter, so total circuit resistance $= (R + r_L)$
- (5) Total voltage across the circuit is : $V_S = I[R + r_L + j(\omega L - 1/\omega C)] = I[R + r_L + j(X_L - X_C)]$

$$= I (R+r_L+jX)=IZ$$

(6) Power consumed in the choke coil $=P_L=I^2(r_L)=V_L I \cos\Phi$

(7) Power factor of the circuit $\cos\Phi = (R + r_L) / Z$

(8) Power consumed in the circuit, $P_t = I^2 (R + r_L) = V_s I \cos\Phi$ (the extra power $I^2 r_L$ is consumed by choke coil)

(9) Power factor of the choke coil $= r_L / \sqrt{r_L^2 + X^2} = P_L / V_L I$

Where

$X_L = \omega L$; Inductive reactance in ohms;

$\omega = 2\pi f$ in radians (f is frequency in HZ) ;

Now, impedance $Z = \sqrt{(R + r_L)^2 + X^2}$

$X_C = (1/\omega C)$; Capacitive Reactance in ohms;

$X = X_L - X_C$, the combined reactance in ohms

Procedure:

- Connect the experimental set as shown in the circuit diagram.
- Select AC 130volt from the supply panel and switch on the input supply.
- Measure voltage drop across each component with the help of voltmeter.
- Measure current flowing in the circuit with the help of ammeter.
- Keep SPDT switch at position 1, Wattmeter will give the power consumed (P_L) in the choke coil.
- Shift SPDT switch to position 2, wattmeter will give the power consumed (P_t) by the total circuit.
- Record the readings of the instruments carefully in the observation table.

Precautions:

- Always keep the measuring instruments in horizontal position.
- Select appropriate range of the instruments i.e the range of the instruments should always be more than the existing value of current or voltage in the circuit .
- Do not touch the resistance as it might have been heated up.

Observation Table:

Sr. No.	Applied voltage	Circuit current	Voltage drop across circuit elements			Power consumed (W)	
	V_s	I	Resistance V_R	Choke coil V_L	Capacitor V_C	Across choke coil P_L	Whole circuit P_t
1.	129.5	0.54A	110V	45.5V	86.2V	6W	67W

Report:

- Using the relations given in theory, calculate the following for supply voltage; Impedance of coil Z_L , Inductive reactance of coil X_L , Capacitive reactance X_C and hence R, L & C.
- Calculate the value of power and power factor of the total circuit and that of choke coil. Compare these values with the wattmeter readings.
- Draw the phasor diagram for any one of the observations.
- Draw the waveform for voltage and current in the RL series circuit as a function of time.

Points to remember:

1. Multiplication factor of wattmeter = $(\text{Voltage range} \times \text{Current range} \times \text{pf of wattmeter}) / \text{Max scale deflection}$.
2. Actual reading of wattmeter = multiplication factor * reading of wattmeter.

Calculations:

Calculations-

Multiplying factor of wattmeter

⇒ Voltage range current range * Power factor

$$= \frac{150 \times 1 \times 1}{75} = 2$$

1. $V_R = I_R = 110 = \frac{0.54}{A} \quad R \Rightarrow 203.70 \Omega$

2. $V_L = I \times L$

$$\frac{V_L}{I} = X_L = \frac{45.5}{0.54} = 84.26 \Omega$$

$$\frac{45.54}{0.54} = L \omega$$

$$L = \frac{45.5}{0.54 \times 3.14 \times 100} = 267.7 \text{ mH}$$

3. $V_C = \frac{I}{f \omega C}$

$$\frac{V_C}{I} = X_C = \frac{86.2}{0.54} = 159.63 \Omega$$

$$\frac{I}{\omega C} = 86.2$$

$$\omega C = \frac{0.54}{86.2 \times 3.14 \times 100} = 19.95 \mu\text{F}$$

4. $P_L = I^2 R_L$

$$\frac{6}{(0.54)^2} = R_L = 20.570 \Omega$$

$$\begin{aligned}
 5 \quad Z &= \sqrt{(R+R_L)^2 + (X_L - X_C)^2} \\
 &= \sqrt{(203.7 + 20.576)^2 + (84.26 - 154.63)^2} \quad (X_C > X_L) \\
 Z &= 236.60
 \end{aligned}$$

$$6 \quad V_S = I \times Z = 0.54 \times 236.60 = 127.764 \text{ V}$$

$$\begin{aligned}
 7 \quad \text{PF of circuit} &= \frac{R+R_L}{Z} = \frac{203.7 + 20.576}{236.60} = \frac{224.276}{236.60} \\
 &= 0.948
 \end{aligned}$$

$$\begin{aligned}
 8 \quad \text{Power consumed in choke coil} &\Rightarrow P_L = V_L I \cos \phi = I^2 R_L \\
 &= (0.54)^2 \times 20.576 = 6 \text{ W}
 \end{aligned}$$


$$9 \quad \text{P.F. of the choke coil} \Rightarrow \frac{R_L}{\sqrt{R_L^2 + X_L^2}} = \frac{P_L}{V_L I} = \frac{6}{45.5 \times 0.54} = 0.2442$$

$$10 \quad \text{Power consumed by whole circuit} \Rightarrow P_t = I^2 (R + R_L) = V_S I \cos \phi$$

$\cos \phi$ is angle b/w V_S & I


$$\phi = \cos^{-1}(0.948)$$
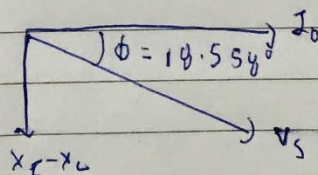
$$127.764 \times 0.54 \times 0.948 = 65.40 \text{ W}$$



$\left\{ \begin{array}{l} X_C > X_L \\ \text{current lags voltage} \end{array} \right.$

Wave form (on RL series circuit)

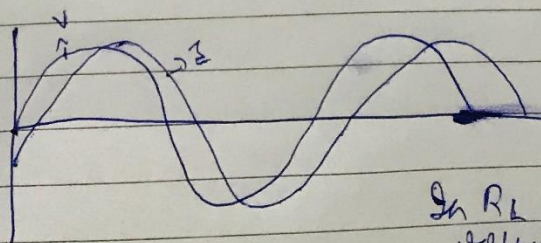

On RL series \rightarrow current lags voltage.

Conclusion- We can see that calculated values of power and power factor are equal or nearly equal to observed values.

Ayush Nagpure