

NAME-Ayush Nagpure

BATCH-2024

SUBGROUP-1H3

ROLL NUMBER-102016100


Experiment: Single Phase AC Parallel Circuit

Objective: To determine experimentally:

1. Current distribution in a single phase AC parallel circuit.
2. Power and power factor of the circuit.
3. The value of circuit elements R, L & C.

Equipment: (1) Voltmeter: 150V AC (2) Ammeter: 3 Amp AC
(3) Wattmeter: 250V, 3 Amp (4) Resistor, Choke coil and Capacitor

Circuit Diagram:

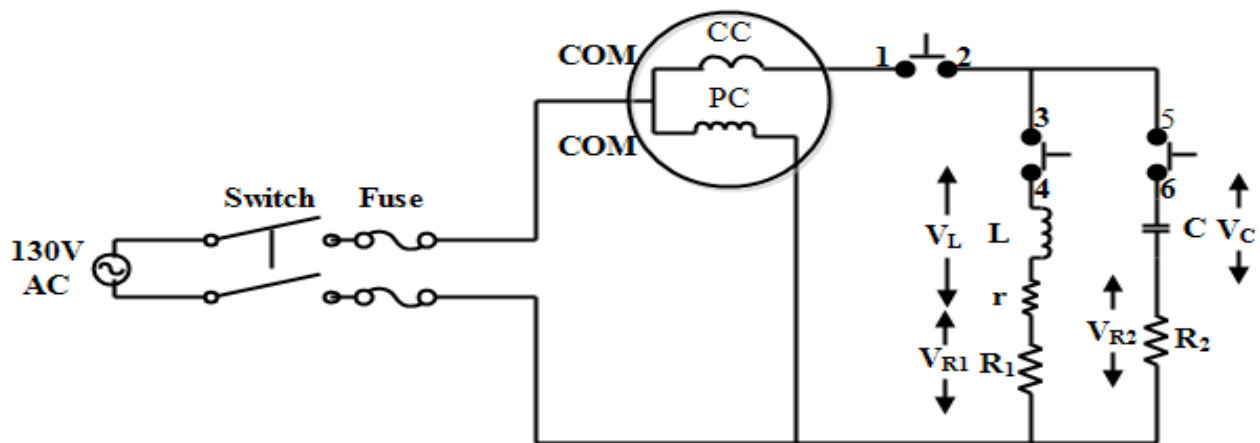

Theory: For a given AC parallel circuit, when energized from an AC source, same voltage drops across all parallel connected branches consisting of resistances R_1 , choke coil L and capacitor C .

For a given ac current I passing through R , L & C ; the voltage drop across

Resistance, $V_R = IR$,

Pure Inductance, $V_L = I(j\omega L)$,

Pure capacitance, $V_C = \frac{I}{j\omega C} = IX_c$

Power dissipated in branch one (RL) for parallel circuit shown in above figure.

1) $P_{RL} = I_1^2(R_1 + r) = V_s I_1 \cos\theta_1$, Power dissipated in branch two (RC)

2) $P_{RC} = I_2^2 R_2 = V_s I_2 \cos\theta_2$, Total power is $P_1 + P_2 = V_s I \cos\theta = P_t$, Total current $I = I_1 + I_2$ (phasor sum)

3) θ_1 , θ_2 and θ are phase angles between supply voltage and current I_1 , I_2 and I respectively. R_1, R_2 are the resistances of rheostats connected in branch 1, 2. V_s is the supply voltage.

Power factor of parallel circuit, $\cos\theta = \frac{I_1 \cos\theta_1 + I_2 \cos\theta_2}{I} = \frac{P_t}{V_s I}$

$$\cos\theta_1 = \frac{P_{RL}}{V_s I_1} = \frac{R_1 + r}{\sqrt{(R_1 + r)^2 + X_L^2}}$$

$$\cos\theta_2 = \frac{P_{RC}}{V_s I_2} = \frac{R_2}{\sqrt{R_2^2 + X_C^2}}$$

Voltage across resistor $R_1, V_{R1} = I_1 R_1$; Voltage across resistor $R_2, V_{R2} = I_2 R_2$

Voltage across inductor $L, V_L = I_1(r + jX_L)$; Voltage across capacitor $C, V_C = I_2(-jX_C)$

Procedure:

- Connect the experiment set up as shown in the circuit diagram
- Select AC 130 Volt from the supply panel and switch on the supply.
 - (case -1) W_1 = power dissipated in RL branch, keeping switches 1-2 & 3-4 closed, 5-6 open.
 - (case -2) W_2 = power dissipated in RC branch, keeping switches 1-2 & 5-6 closed, 3-4 open.
 - (case -3) W = Total power consumed in circuit = $W_1 + W_2$, (all switches closed).
- Similarly measure current I_1 , I_2 and I with help of current measurement board.
- Record the readings of the instruments carefully.

Precautions:

- Always keep measuring instruments in horizontal position. i.e. table mode.
- Select appropriate range of the instruments. i.e. the range of the instruments should always be more than the existing value of current or voltage in the circuit.
- Don't touch the resistance even after switching off the supply as it might have been heated up.

Observations:

CASE	Supply (V _s)	Voltage across elements				Current through switch			Power consumed		
		V _{R1}	V _{R2}	V _L	V _C	1-2 I	3-4 I ₁	5-6 I ₂	W ₁ P _{RL}	W ₂ P _{RC}	W P _t
Case 1	129V	108V	98V	44V	78V	0.91A	0.53A	0.48A	64W	40W	112W
Case 2											
Case 3											

Report:

- Using various relations, calculate R₁, R₂, X_L, X_C, L, C assuming the supply frequency as 50Hz.
- Calculate the value of power and power factor of the circuit from above parameters.
- Draw the phasor for one reading when both switches 5-6 and 3-4 are closed.
- What will be the nature of lagging and leading power factor loads? Draw the position of voltage and current phasor for these loads.

Points to remember:

1. Multification factor of watt meter used = (Voltage range * Current range * pf of wattmeter) / Max scale deflection
2. Actual reading of wattmeter = multification factor * reading of wattmeter

CALCULATIONS:

CALCULATIONS

$$\text{Multiplication factor} = \frac{\text{Voltage range} \times \text{Current range} \times \text{Power factor}}{\text{Max. scale deflection}}$$

$$\rightarrow \frac{250 \times 2.5 \times 1}{156.25} = 4$$

Observed Power

$$P_t \rightarrow 28W = 28 \times \text{Multiplication factor} = 28 \times 4 \Rightarrow 112W$$

$$P_{RC} \rightarrow 10W = 10 \times 4 \Rightarrow 40W$$

$$P_{RL} \rightarrow 16W = 16 \times 4 = 64W$$

Calculated

$$V_{R_1} = I_1 \times R_1 \Rightarrow R_1 = \frac{V_{R_1}}{I_1} \Rightarrow \frac{103}{0.53A} \Rightarrow 203.773 \Omega$$

$$X_L \Rightarrow \frac{V_L}{I_1} \Rightarrow \frac{44}{0.53} \Rightarrow 83.01 \Omega$$

$$X_L = L\omega \Rightarrow \frac{83.01}{3.14 \times 2 \times 50} = L \quad \left\{ \begin{array}{l} 50\text{Hz} = \text{freq.} \\ 2\pi f = \omega \end{array} \right.$$
$$\Rightarrow 0.2643\text{H} = 264.3\text{mH}$$

$$V_{R_2} \Rightarrow I_2 \times R_2 \quad R_2 = \frac{V_{R_2}}{I_2} \Rightarrow \frac{98}{0.48} = 204.166$$

$$X_C \Rightarrow \frac{V_C}{I_2} \Rightarrow \frac{78}{0.48} = 162.5 \Omega$$

$$X_C = \frac{1}{C\omega} \quad C = \frac{1}{162.5 \times 314} = \frac{1}{51025}$$
$$\Rightarrow 19.6 \mu\text{F}$$

$$Z_1 \Rightarrow \sqrt{(R_1)^2 + (X_L)^2}$$

$$\Rightarrow \sqrt{(203.773)^2 + (83.01)^2}$$
$$\Rightarrow \sqrt{41523.43553 + 6890.6601} = \sqrt{48414.095}$$
$$= 220.032 \text{ ohm}$$

$$Z_2 = \sqrt{(R_2)^2 + (X_C)^2} = \sqrt{(204.166)^2 + (162.5)^2}$$

Capacitor branch

$$= \sqrt{41683.7556 + 26406.25}$$

$$= \sqrt{68090.0056} = 260.940 \Omega$$

$$\cos \theta_2 \rightarrow \frac{R_2}{Z_2} \rightarrow \frac{204.166}{260.940} = 0.782425$$

$$\theta_2 = 38.51^\circ$$

$$\cos \theta_1 \rightarrow \frac{R_1}{Z_1} \rightarrow \frac{202.773}{220.032} \rightarrow 0.9261062$$

$$\theta_1 = \cos^{-1}(0.9261) \rightarrow 22.1657$$

$$\lambda = \sqrt{(\cos \theta_1 \times Z_1) \times R_1} \rightarrow (0.9261 \times 220.032) \times 202.773$$

$$P_1 \rightarrow \frac{P_{RL}}{I_1^2} - R_1 \rightarrow \frac{64}{(0.53)^2} - 203.773$$

$$\rightarrow \frac{64}{0.2809} - 203.773$$

$$227.833 - 203.773 = 24 \Omega$$

$$P_2 \rightarrow I_2^2 (R_2) \rightarrow (0.48)^2 \times 204.166 = 47.04 \text{ W}$$

$$P_1 \rightarrow P_{RL} \rightarrow I_1^2 (R_1 + R_2) \rightarrow (0.53)^2 (203.773 + 24)$$



$$\rightarrow 62.98 \approx 64 \text{ W}$$

$$P_t = P_1 + P_2 = 47.04 + 64 = 111.04$$

Nature of lagging and leading power factor.

→ lagging p.f. (Inductive nature)

→ leading p.f. (Capacitive nature)

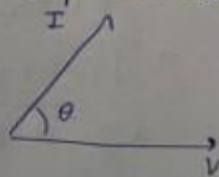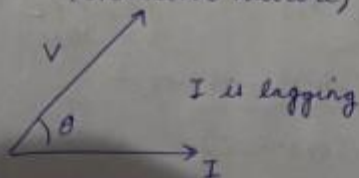

Results.

$$R_1 \rightarrow 203.773 \Omega$$

$$R_2 \rightarrow 204.116 \Omega$$

$$C = 19.6 \mu F$$

$$R = 24 \Omega$$

$$X_C \rightarrow 162.5 \Omega$$

$$\cos \theta_2 = 0.782425$$

$$P_1 = P_{RL} = 64 W$$

$$P_2 = P_{RC} = 47.04 W$$

$$P_t \rightarrow 111.04 W$$

$$Z_1 \rightarrow 220.032 \Omega$$

$$Z_2 \rightarrow 260.940 \Omega$$

$$L \rightarrow 264.3 mH$$

$$X_L \rightarrow 83.01 \Omega$$

$$\cos \theta_1 \rightarrow 0.92621^\circ$$

CONCLUSION: We can see that the calculated values of power and power factor are equal or nearly equal to observed values.

Ayush Nagpure