

Ayush Nagpure Batch – 2024 Application No - 158377
Subgroup – 1H3

Experiment: To study the Thevenin's Theorem

Objective: To verify the Thevenin's Theorem.

Apparatus: Virtual using Tinkercad (www.tinkercad.com)

Theory:

This circuit states that the current in any bilateral circuit element (R_L) in a network is the same as would be obtained if that circuit element (R_L) is supplied with a source Voltage in series with an equivalent resistance R_{th} being the open circuit voltage at the terminals from which R_L has been removed and R_{th} being the resistance that would be measured at these terminals after all sources have been replaced by their internal resistance respectively. According to this theorem, if resistance R_L be connected between two terminals in a linear bilateral network, then resulting steady state current through resistor will be $V_{th}/(R_L + R_{th})$, where V_{th} is the potential difference between points A and B after removing R_L such that for network shown in figure.

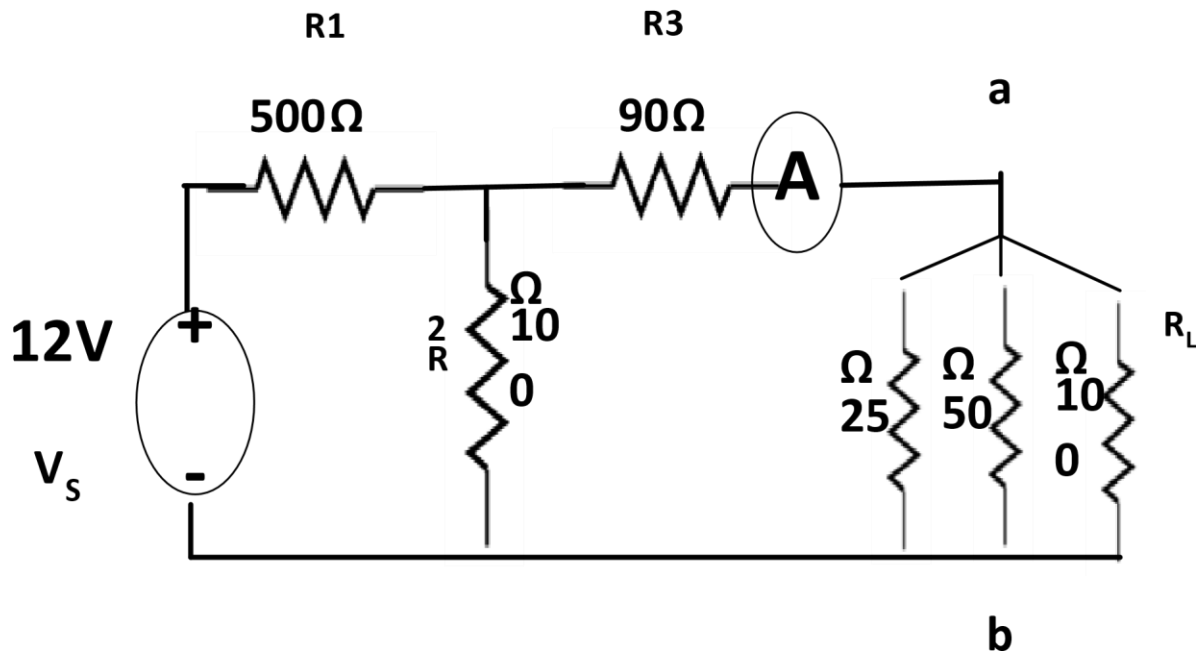


Fig. Circuit diagram for verification of Thevenin's Theorem

$V_{th} = V \cdot R_2 / (R_1 + R_2)$ And Thevenin's resistance measured between terminals ab (with source removed and replaced by its internal resistance if any, otherwise replace by short circuit) is given by: $R_{th} = [R_1 \cdot R_2 / (R_1 + R_2)] + R_3$

Now external resistance R_L is connected between terminals ab such that Thvenin's equivalent circuit for the network will be as shown in figure. Current through R_L will be


$$I_L = V_{th} / (R_{th} + R_L)$$



Procedure:




1. Connect the circuit as shown in the circuit diagram on tinkercad workspace. Once the circuit is made take a snapshot and paste in the manual.
2. To verify the theorem, measure Thevenin resistance by removing the load and deactivating the sources in the circuit.
3. Remove R_L from the circuit and measure the open circuit voltage V_{th} across the end points by a DC voltmeter.
4. Once R_{th} and V_{th} are know, draw the Thevenin's equivalent circuit.

- Observation table:**


Circuit diagram on Tinkercad:

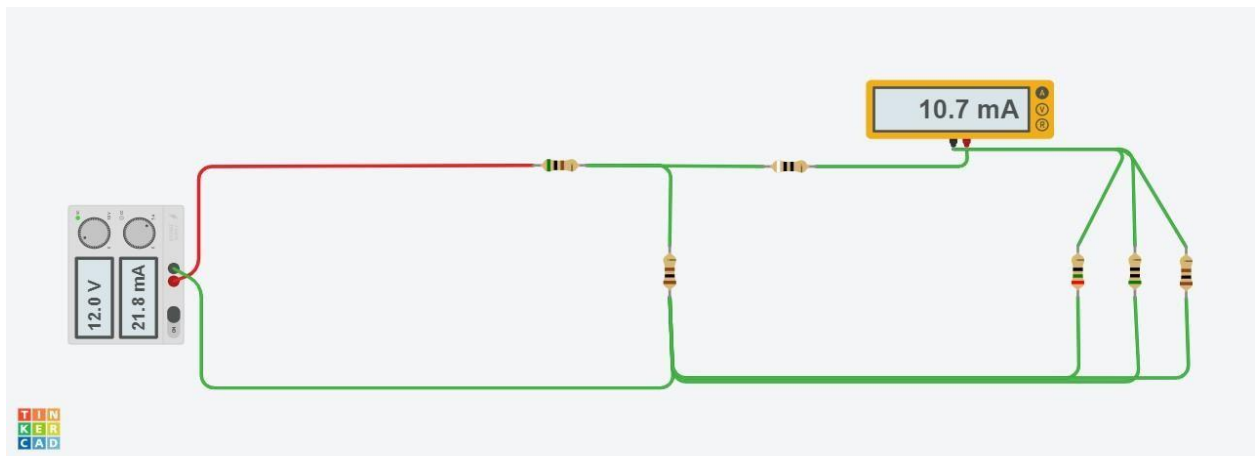

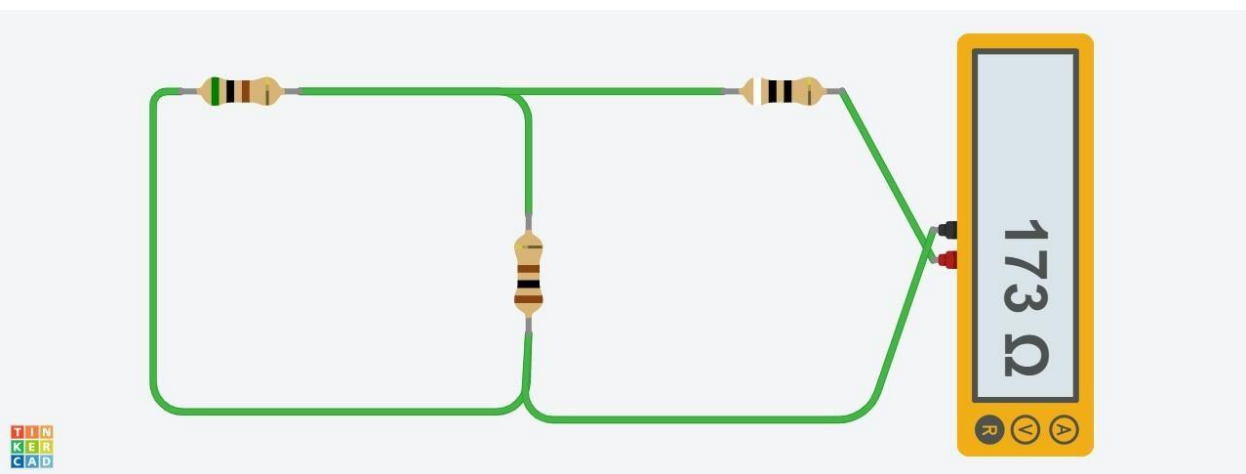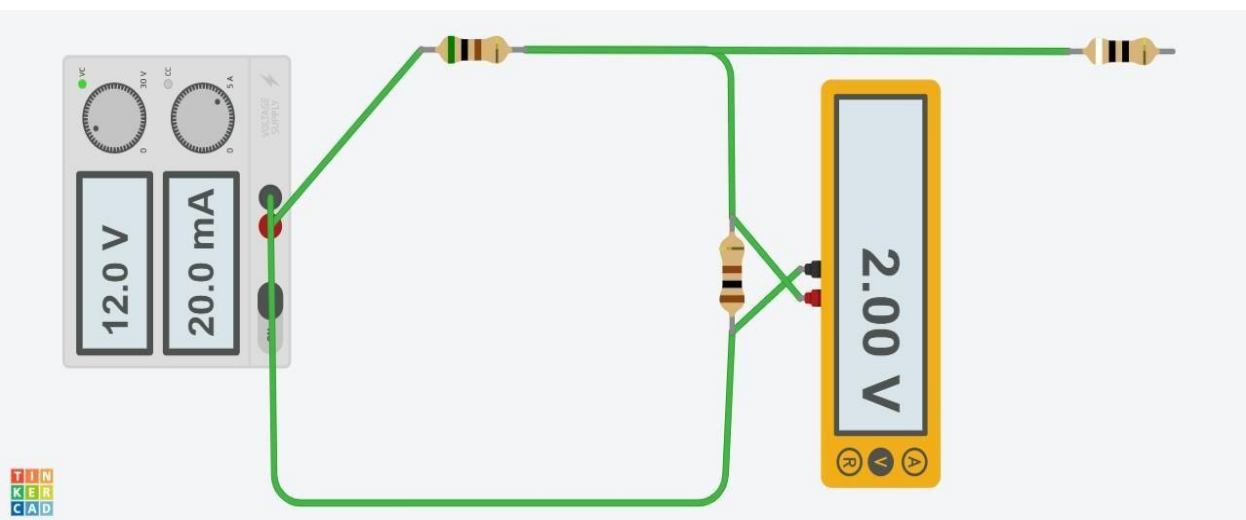

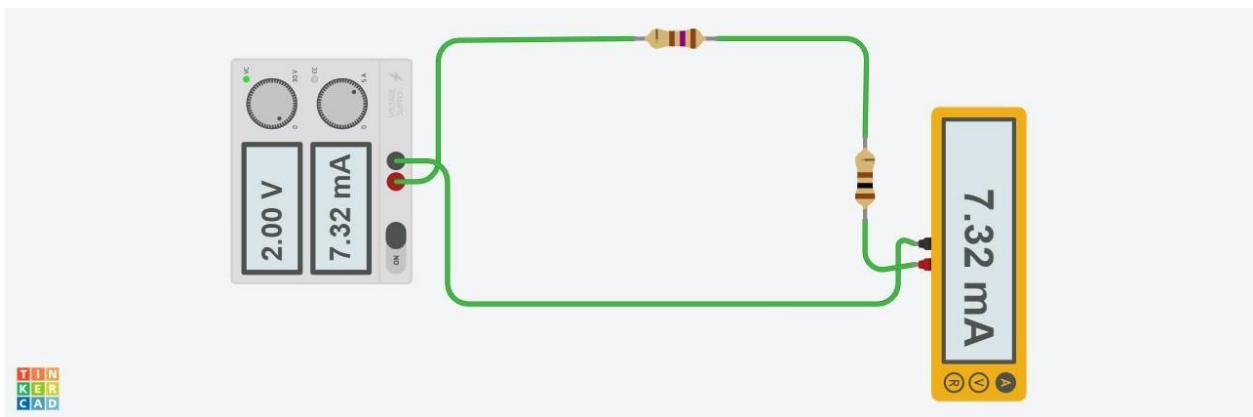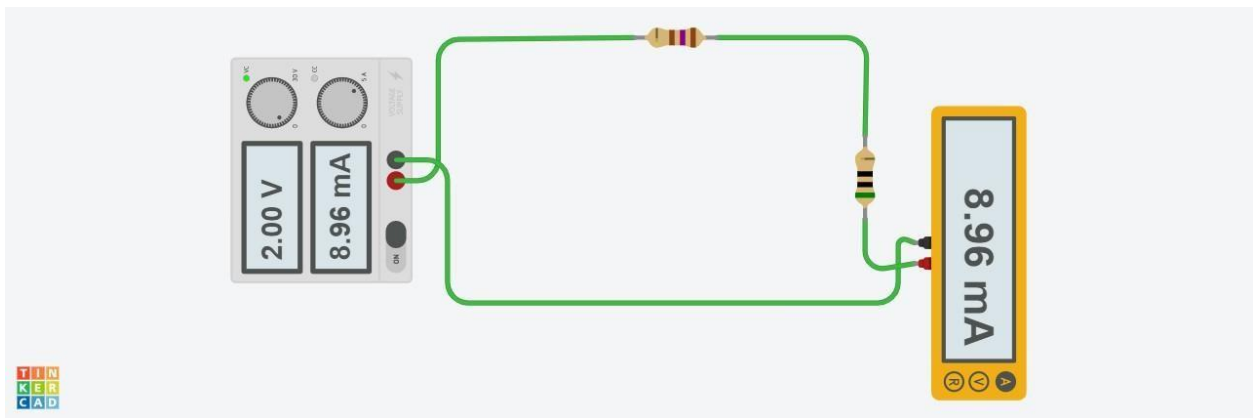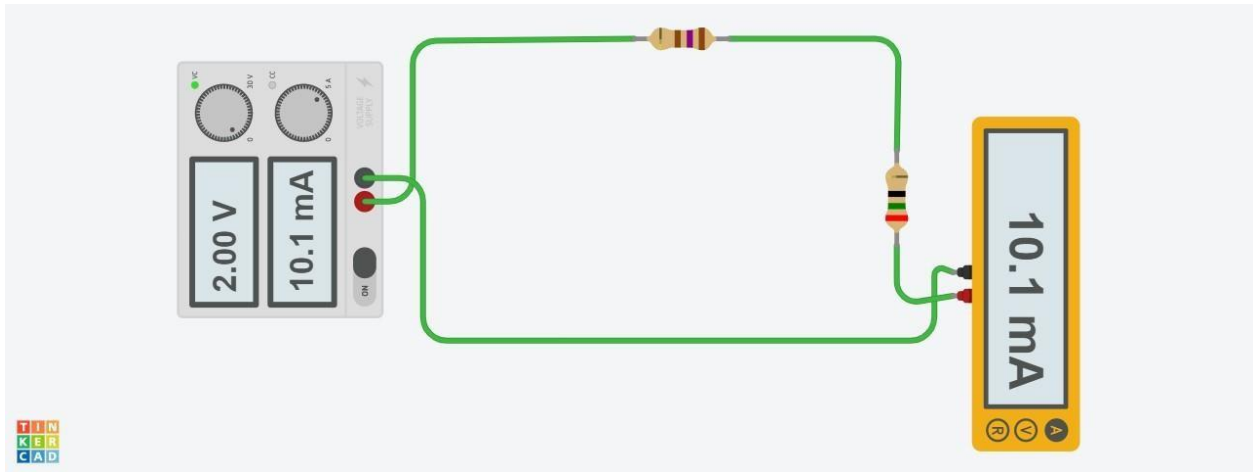


Calculations:

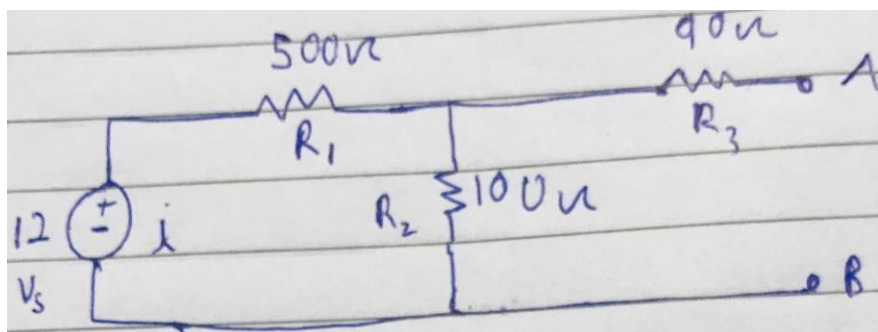

$$i = \frac{12}{(500 + 100)} = \frac{12}{600} = 0.02 \text{ A}$$
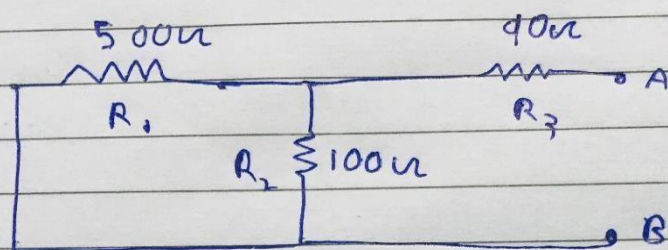
$$= i \times R_2 = 0.02 \times 100 = \underline{2 \text{ V}}$$




R_1 & R_2 are in parallel

$$R' = \frac{1}{\frac{1}{500} + \frac{1}{100}} = \frac{500 \times 100}{600} = 83.3 \Omega$$


R' is in series with R_3
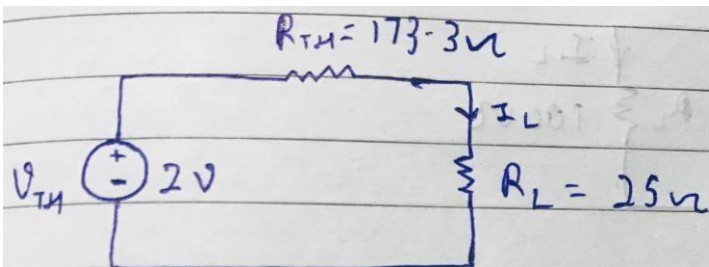
$$R_{eq} \quad R_{in} = 83.3 + 40 = 123.3 \Omega$$




$$I_L = \frac{V_{TH}}{(R_{TH} + R_L)} = \frac{2}{173.3 + 25} = 0.0101A = 10.01mA$$
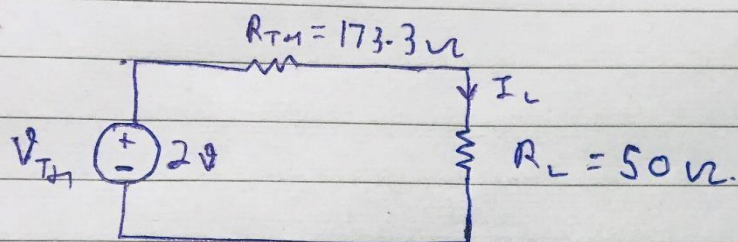
$$\% \text{ Error} = \left(\frac{10.1 - 10.01}{10.1} \right) \times 100 = 0.89\%$$



$$I_L = \frac{V_{TH}}{(R_{TH} + R_L)} = \frac{2}{(173.3 + 50)} = 8.95mA$$
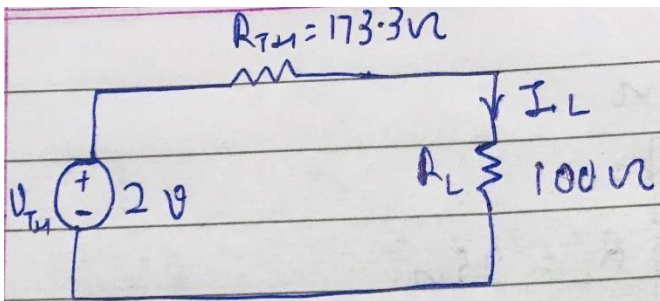
$$\% \text{ Error} = \left(\frac{8.96 - 8.95}{8.96} \right) \times 100 = 0.112\%$$



$$I_L = \frac{2}{173.3 + 100} = 7.31 \text{ mA}$$

$$\therefore \text{Error} = \left(\frac{7.32 - 7.31}{7.32} \right) \times 100 = 0.26\%$$

Conclusion: Hence Thevenin's Theorem is verified.