

Experiment: To study the Thevenin's Theorem

Objective: To verify the Thevenin's Theorem.

Apparatus: Virtual using Tinkercad (www.tinkercad.com)

Theory:

This circuit states that the current in any bilateral circuit element (R_L) in a network is the same as would be obtained if that circuit element (R_L) is supplied with a source Voltage in series with an equivalent resistance R_{th} being the open circuit voltage at the terminals from which R_L has been removed and R_{th} being the resistance that would be measured at these terminals after all sources have been replaced by their internal resistance respectively. According to this theorem, if resistance R_L be connected between two terminals in a linear bilateral network, then resulting steady state current through resistor will be $V_{th}/(R_L + R_{th})$, where V_{th} is the potential difference between points A and B after removing R_L such that for network shown in figure.

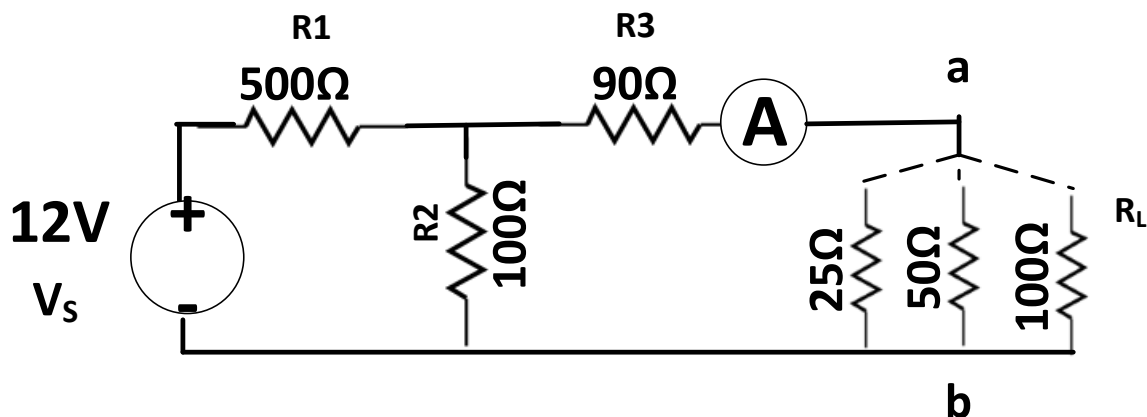


Fig. Circuit diagram for verification of Thevenin's Theorem

$$V_{th} = V * R_2 / (R_1 + R_2)$$

And Thevenin's resistance measured between terminals ab (with source removed and replaced by its internal resistance if any, otherwise replace by short circuit) is given by:

$$R_{th} = [R_1 * R_2 / (R_1 + R_2)] + R_3$$

Now external resistance R_L is connected between terminals ab such that Thvenin's equivalent circuit for the network will be as shown in figure. Current through R_L will be

$$I_L = V_{th} / (R_{th} + R_L)$$

Procedure:

1. Connect the circuit as shown in the circuit diagram on tinkercad workspace. Once the circuit is made take a snapshot and paste in the manual.
2. To verify the theorem, measure Thevenin resistance by removing the load and deactivating the sources in the circuit.
3. Remove R_L from the circuit and measure the open circuit voltage V_{th} across the end points by a DC voltmeter.
4. Once R_{th} and V_{th} are know, draw the Thevenin's equivalent circuit.
5. Now measure current I_L by selecting the load resistance of 25, 50 and 100 Ω respectively by the multimeter.
6. Again find the Thevenin equivalent of the circuit theoretically and compare it with the simulation readings.

Observation table:

S. No.	Load resistance	V_{th}	R_{th}	I_L	Theoretical I_L	% Error
1						
2						
3						

Circuit diagram on Tinkercad:

(paste here)

Calculations:**Conclusion:**