

Experiment: BJT CE Mode

Aim: To obtain Input and Output Characteristics of Bipolar Junction Transistor in Common Emitter Mode

Apparatus: Online (using Virtual Lab (<http://vlabs.iitkgp.ernet.in/be/>)

Theory:

A bipolar junction transistor, BJT, is a single piece of silicon with two back-to-back P-N junctions. BJTs can be made either as PNP or as NPN.

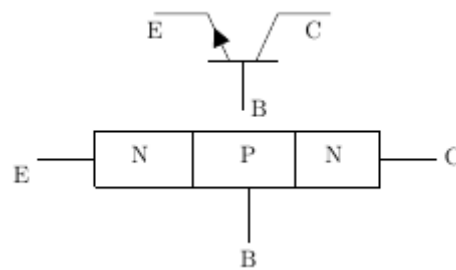


Figure 1: Structures, layers and circuit symbol of NPN transistor

They have three regions and three terminals, emitter, base, and collector represented by E, B, and C respectively. The direction of the arrow indicates the direction of the current in the emitter when the transistor is conducting normally. An easy way to remember this is NPN stands for "Not Pointing iN".

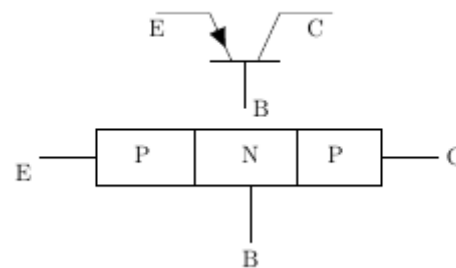


Figure 2: Structures, layers and circuit symbol of PNP transistor

Emitter (E): It is the region to the left end which supply free charge carriers i.e., electrons in n-p-n or holes in p-n-p transistors. These majority carriers are injected to the middle region i.e. electrons in the p region of n-p-n or holes in the n region of p-n-p transistor. Emitter is a heavily doped region to supply a large number of majority carriers into the base.

Base (B): It is the middle region where either two p-type layers or two n-type layers are sandwiched. The majority carriers from the emitter region are injected into this region. This region is thin and very lightly doped.

Collector (C): It is the region to right end where charge carriers are collected. The area of this region is largest compared to emitter and base region. The doping level of this region is intermediate between heavily doped emitter region and lightly doped base region.

Cutoff Region: Base-emitter junction is reverse biased. No current flow.

Saturation Region: Base-emitter junction is forward biased and Collector-base junction is forward biased.

Active Region: Base-emitter junction forward biased and Collector-base junction is reverse biased.

Procedure:

1. BJT Common Emitter - Input Characteristics

(http://vlabs.iitkgp.ernet.in/be/exp11/bjtcein_ver1.html)

1. Initially set rheostat $R_{h1} = 1 \Omega$ and rheostat $R_{h2} = 1 \Omega$
2. Set the Collector-Emitter Voltage(V_{CE}) to 1 V by adjusting the rheostat R_{h2}
3. Base Emitter Voltage(V_{BE}) is varied by adjusting the rheostat R_{h1} .
4. Note the reading of Base current(I_B) in micro Ampere.
5. Click on 'Plot' to plot the I-V characteristics of Common-Emitter configuration. A graph is drawn with V_{BE} along X-axis and I_B along Y-axis.
6. Click on 'Clear' button to take another sets of readings
7. Now set the Collector-Emitter Voltage(V_{CE}) to 2 V, 3 V, 4 V

2. BJT Common Emitter - Output Characteristics

(http://vlabs.iitkgp.ernet.in/be/exp11/bjtceop_ver1.html)

1. Initially set rheostat $R_{h1} = 1 \Omega$ and rheostat $R_{h2} = 1 \Omega$
2. Set the Base current(I_B) 15 μA by adjusting the rheostat R_{h1}
3. Vary the Collector-Emitter Voltage(V_{CE}) is varied by adjusting the rheostat R_{h2} .
4. Note the reading of Collector current(I_C).
5. Click on 'Plot' to plot the I-V characteristics of Common-Emitter configuration. A graph is drawn with V_{CE} along X-axis and I_C along Y-axis.
6. Click on 'Clear' button to take another sets of readings
7. Now set the Base Current(I_B) to 20 μA

Circuit Diagram:

Paste the circuit diagram for (take snapshot from vlab)

1. BJT CE Input Characteristics
2. BJT CE Output Characteristics

Observation Table:*BJT CE Input Characteristics*

$V_{CE} =$		
S. No.	V_{BE}	I_B

BJT CE Output Characteristics

$I_B =$		
S. No.	V_{CE}	I_C

Results:*Paste the graphs for*

1. *BJT CE Input Characteristics*
2. *BJT CE Output Characteristics*

Conclusion: